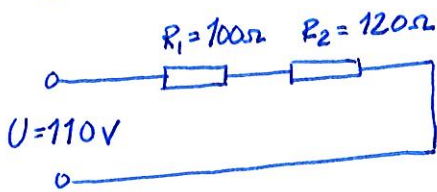


3.0 KOPLINGER MED RESISTANSER OG ELEMENTER

3.1 SERIEKOPLING

3.1.1




$$R_T = R_1 + R_2 = 100\Omega + 120\Omega = \underline{\underline{220\Omega}}$$

$$I = \frac{U}{R_T} = \frac{110V}{220\Omega} = \underline{\underline{0,5A}}$$

$$\Delta U_1 = I \cdot R_1 = 0,5A \cdot 100\Omega = \underline{\underline{50V}}$$

$$\Delta U_2 = I \cdot R_2 = 0,5A \cdot 120\Omega = \underline{\underline{60V}}$$

3.1.2

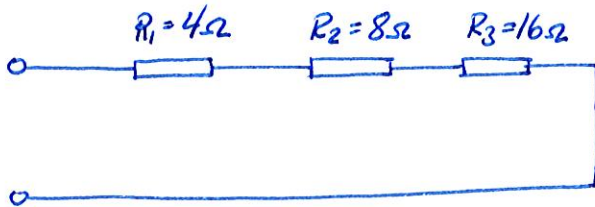

$$R_T = R_1 + R_2 + R_3 = 4\Omega + 8\Omega + 16\Omega = \underline{\underline{28\Omega}}$$


$$I = \frac{U}{R_T} = \frac{100V}{28\Omega} = \underline{\underline{3,57A}}$$

$$\Delta U_1 = I \cdot R_1 = 3,57A \cdot 4\Omega = \underline{\underline{14,3V}}$$

$$\Delta U_2 = I \cdot R_2 = 3,57A \cdot 8\Omega = \underline{\underline{28,6V}}$$

$$\Delta U_3 = I \cdot R_3 = 3,57A \cdot 16\Omega = \underline{\underline{57,1V}}$$

3.1.3

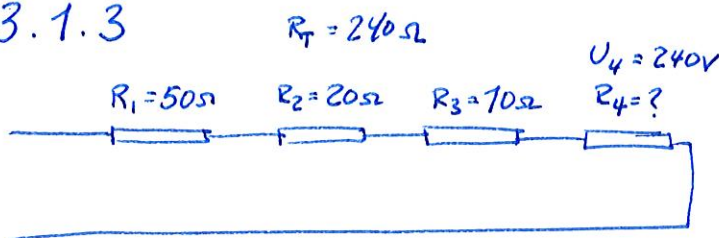

$$a) R_T = R_1 + R_2 + R_3 + R_4$$

$$R_4 = R_T - (R_1 + R_2 + R_3)$$

$$R_4 = 240\Omega - (50\Omega + 20\Omega + 10\Omega) = \underline{\underline{160\Omega}}$$

$$b) I = \frac{U_4}{R_4} = \frac{240V}{160\Omega} = \underline{\underline{1,5A}}$$

$$c) U = I \cdot R_T = 1,5A \cdot 240\Omega = \underline{\underline{360V}}$$

$$\Delta U_1 = I \cdot R_1 = 1,5A \cdot 50\Omega = \underline{\underline{75V}}$$

$$\Delta U_2 = I \cdot R_2 = 1,5A \cdot 20\Omega = \underline{\underline{30V}}$$

$$\Delta U_3 = I \cdot R_3 = 1,5A \cdot 10\Omega = \underline{\underline{15V}}$$


$$d) P = U \cdot I = 360V \cdot 1,5A = \underline{\underline{540W}}$$

$$P_1 = \Delta U_1 \cdot I = 75V \cdot 1,5A = \underline{\underline{112,5W}}$$

$$P_2 = \Delta U_2 \cdot I = 30V \cdot 1,5A = \underline{\underline{45W}}$$

$$P_3 = \Delta U_3 \cdot I = 15V \cdot 1,5A = \underline{\underline{22,5W}}$$

3.1.4

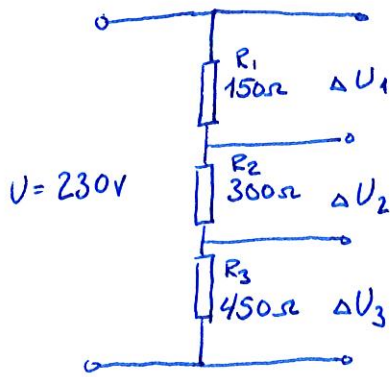

$$R_T = R_1 + R_2 + R_3 = 150\Omega + 300\Omega + 450\Omega = \underline{900\Omega}$$

$$I = \frac{U}{R_T} = \frac{230V}{900\Omega} = \underline{0,256A}$$

$$\Delta U_1 = I \cdot R_1 = 0,256A \cdot 150\Omega = \underline{38,3V}$$


$$\Delta U_2 = I \cdot R_2 = 0,256A \cdot 300\Omega = \underline{76,7V}$$

$$\Delta U_3 = I \cdot R_3 = 0,256A \cdot 450\Omega = \underline{115V}$$

$$\Delta U_{12} = \Delta U_1 + \Delta U_2 = 38,3V + 76,7V = \underline{115V}$$

$$\Delta U_{23} = \Delta U_2 + \Delta U_3 = 76,7V + 115V = \underline{191,7V}$$

3...5

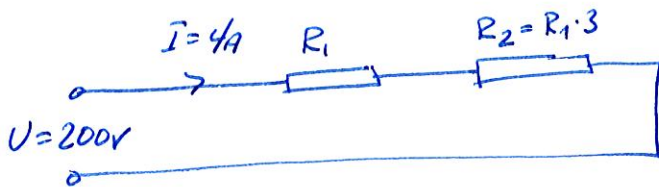

$$R_T = \frac{U}{I} = \frac{200V}{4A} = \underline{50\Omega}$$

a)

$$R_T = R_1 + R_2 = R_1 + R_1 \cdot 3$$

$$50\Omega = R_1 + R_1 \cdot 3$$

$$50\Omega = R_1(1+3)$$

$$\frac{50\Omega}{4} = R_1$$

$$R_1 = \underline{12,5\Omega}$$

$$R_T = R_1 + R_2$$

$$50\Omega = 12,5\Omega + R_2$$

$$R_2 = 50\Omega - 12,5\Omega = \underline{37,5\Omega}$$

b)

$$I = \frac{U}{R_T} = \frac{150V}{50\Omega} = \underline{3A}$$

$$\Delta U_1 = I \cdot R_1 = 3A \cdot 12,5\Omega = \underline{37,5V}$$

$$\Delta U_2 = I \cdot R_2 = 3A \cdot 37,5\Omega = \underline{112,5V}$$