

# 7.0 RESISTANS - SPOLE - KONDENSATOR

## 7.1 RESISTANS - SPOLE - KONDENSATOR TILKOPLET VEKSELSTRØM ENKELTVIS.

### 7.1.1

$$R = \frac{U}{I} = \frac{230V}{5A} = \underline{\underline{46\Omega}}$$

### 7.1.2

a)  $X_L = 2 \cdot \pi \cdot f \cdot L = 2 \cdot \pi \cdot 50Hz \cdot 63,7 \cdot 10^{-3}H = \underline{\underline{20\Omega}}$

b)  $Z = X_L = \underline{\underline{20\Omega}}$  (for en ideell spole)

$$I = \frac{U}{X_L} = \frac{230V}{20\Omega} = \underline{\underline{11,5A}}$$


### 7.1.3

a)  $X_C = \frac{1}{2 \cdot \pi \cdot f \cdot C} = \frac{1}{2 \cdot \pi \cdot 50Hz \cdot 45,47 \cdot 10^{-6}F} = \underline{\underline{70\Omega}}$

b)  $Z = X_C = \underline{\underline{70\Omega}}$  (for en ideell kondensator)

$$I = \frac{U}{X_C} = \frac{230V}{70\Omega} = \underline{\underline{3,29A}}$$

### 7.1.4

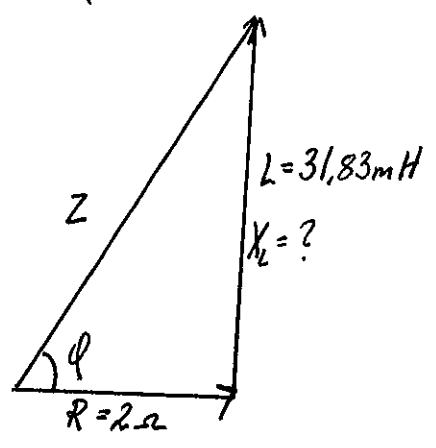

a)  $X_L = 2 \cdot \pi \cdot f \cdot L = 2 \cdot \pi \cdot 50Hz \cdot 31,83 \cdot 10^{-3}H = \underline{\underline{10,0\Omega}}$


b)  $\bar{Z} = R + jX_L = 2\Omega + j10\Omega = \underline{\underline{10,2\Omega}} \angle \phi = \underline{\underline{78,7^\circ}}$   
eller:

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{2^2 + 10^2} = \underline{\underline{10,2\Omega}} \quad \cos\phi = \frac{R}{Z} = \frac{2}{10,2} = \underline{\underline{0,196}}$$
  
$$\angle \phi = \underline{\underline{78,7^\circ}} \quad (\angle \phi = \cos^{-1} 0,196 = 78,7^\circ)$$

c)  $\cos\phi = \cos 78,7^\circ = \underline{\underline{0,196}}$

d)  $I = \frac{U}{Z} = \frac{110V}{10,2\Omega} = \underline{\underline{10,8A}}$

7.1.5

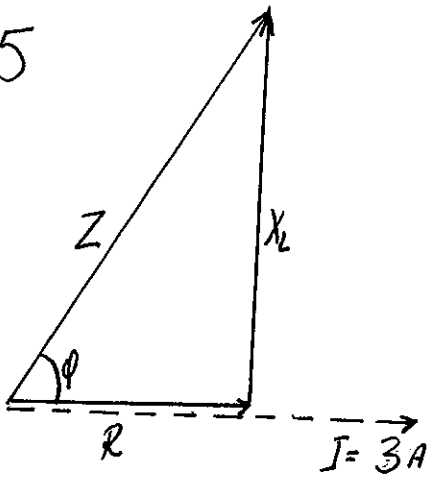a) Likestrøm gir resistansen i spolen:

$$R = \frac{U}{I} = \frac{100V}{20A} = \underline{\underline{5\Omega}}$$

b) Vekselstrøm gir impedansen i spolen:


$$Z = \frac{U}{I} = \frac{210V}{3A} = \underline{\underline{70\Omega}}$$

$$c) X_L = \sqrt{Z^2 - R^2} = \sqrt{70\Omega^2 - 5\Omega^2} = \underline{\underline{69,8\Omega}}$$

$$X_L = 2 \cdot \pi \cdot f \cdot L \quad L = \frac{X_L}{2 \cdot \pi \cdot f} = \frac{69,8\Omega}{2 \cdot \pi \cdot 50\text{Hz}} = \underline{\underline{222,2\text{mH}}}$$

$$d) \cos\phi = \frac{R}{Z} = \frac{5\Omega}{70\Omega} = \underline{\underline{0,0714}} \quad \angle\phi = \underline{\underline{85,9^\circ}}$$

7.1.6

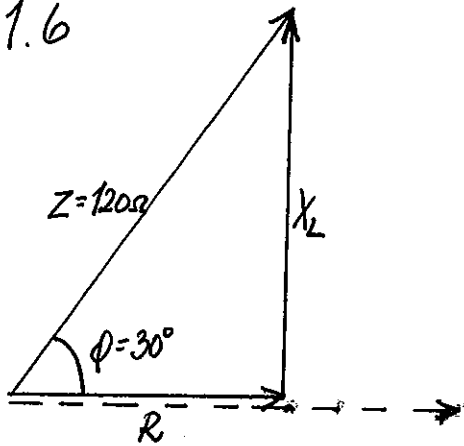

$$a) \cos\phi = \frac{R}{Z}$$

$$R = \cos\phi \cdot Z = \cos 30^\circ \cdot 120\Omega = \underline{\underline{103,9\Omega}}$$

$$\sin\phi = \frac{X_L}{Z}$$

$$X_L = \sin\phi \cdot Z = \sin 30^\circ \cdot 120\Omega = \underline{\underline{60,0\Omega}}$$

$$b) \cos\phi = \frac{R}{Z} = \frac{103,9\Omega}{120,0\Omega} = \underline{\underline{0,866}}$$

$$c) X_L = 2 \cdot \pi \cdot f \cdot L \quad L = \frac{X_L}{2 \cdot \pi \cdot f} = \frac{60,0\Omega}{2 \cdot \pi \cdot 60\text{Hz}} = \underline{\underline{159,2\text{mH}}}$$

7.1.7

$$\bar{Z} = R + jX_L = 13\Omega + j25\Omega = \underline{\underline{28,2\Omega}} \quad \angle\phi = \underline{\underline{62,5^\circ}}$$

### 7.1.8

$$\bar{Z} = Z \angle \varphi = 10 \Omega \angle 53,73^\circ = \underline{\underline{6,0 \Omega + j 8,0 \Omega}}$$

### 7.1.9



- Resistans → Resistans R
- Spole → Selwinduktans L
- Kondensator → kapasitans C

### 7.1.10

$$X_c = \frac{1}{2 \cdot \pi \cdot f \cdot C} = \frac{1}{2 \cdot \pi \cdot 60 \text{ Hz} \cdot 26,52 \cdot 10^{-6} \text{ F}} = \underline{\underline{100 \Omega}}$$

$$I = \frac{U}{X_c} = \frac{440 \text{ V}}{100 \Omega} = \underline{\underline{4,4 \text{ A}}}$$

### 7.1.11

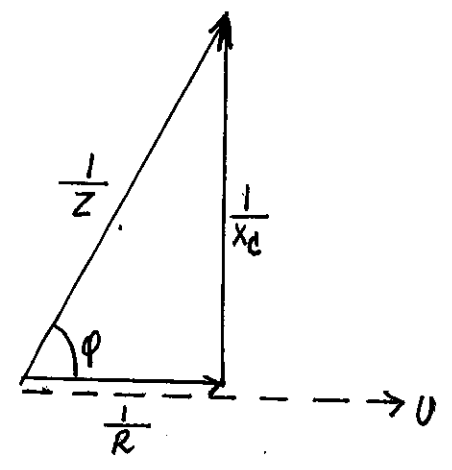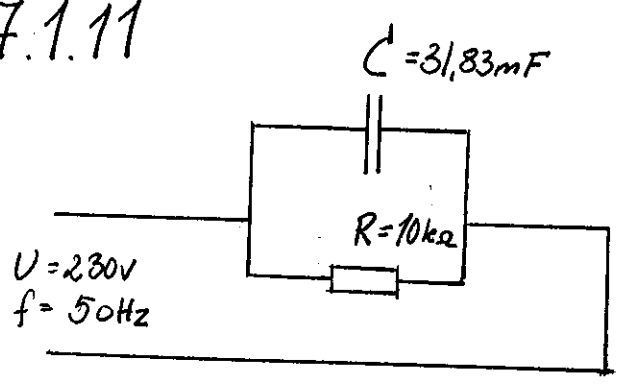

$$X_c = \frac{1}{2 \cdot \pi \cdot f \cdot C} = \frac{1}{2 \cdot \pi \cdot 50 \text{ Hz} \cdot 31,83 \cdot 10^{-3} \text{ F}} = \underline{\underline{100 \Omega}}$$

$$\bar{Z} = \frac{R \cdot jX_c}{R + jX_c} = \frac{10 \cdot 10^3 \Omega \cdot j 100 \Omega}{10 \cdot 10^3 \Omega + j 100 \Omega} = \frac{0 + j 1,0 \cdot 10^6 (\Omega^2)}{10 \cdot 10^3 \Omega + j 100 \Omega} = \frac{1,0 \cdot 10^6 \Omega \angle 90^\circ}{10000,5 \Omega \angle 0,573^\circ}$$

$$\bar{Z} = \underline{\underline{99,99}} \approx \underline{\underline{100 \Omega}}$$

$$\angle \varphi = \angle \varphi_1 - \angle \varphi_2 = 90^\circ - 0,573^\circ = \underline{\underline{89,43^\circ}}$$

7.1.12

$$a) X_C = \frac{1}{2\pi \cdot f \cdot C} = \frac{1}{2 \cdot \pi \cdot 60 \text{ Hz} \cdot 53,05 \cdot 10^{-6} \text{ F}} = \underline{\underline{50,0 \Omega}}$$

$$b) \bar{Z} = \frac{R \cdot jX_C}{R + jX_C} = \frac{7,0 \cdot 10^3 \Omega \cdot j50,0 \Omega}{7,0 \cdot 10^3 \Omega + j50,0 \Omega} = \frac{0 + j0,35 \cdot 10^6 \Omega^2}{7,0 \cdot 10^3 \Omega + j50,0 \Omega} =$$

$$= \frac{350 \cdot 10^3 \Omega \angle 90^\circ}{7000,18 \Omega \angle 0,409^\circ} = \underline{\underline{50,0 \Omega}}$$

$$\angle \varphi = \angle \varphi_1 - \angle \varphi_2 = 90^\circ - 0,409^\circ = \underline{\underline{89,59^\circ}} \quad c) \cos \varphi = \underline{\underline{0,00714}}$$

7.1.13

$$Z = X_C = \frac{U}{I} = \frac{200 \text{ V}}{0,5 \text{ A}} = 400 \Omega$$

$$X_C = \frac{1}{2 \cdot \pi \cdot f \cdot C} \Rightarrow f = \frac{1}{2 \cdot \pi \cdot C \cdot X_C} = \frac{1}{2 \cdot \pi \cdot 23,87 \cdot 10^{-6} \text{ F} \cdot 400 \Omega} = \underline{\underline{16,67 \text{ Hz}}}$$

7.1.14

Likeström:

$$R = \frac{U}{I} = \frac{115 \text{ V}}{30 \text{ A}} = \underline{\underline{3,83 \Omega}}$$

Vekeleström:

$$Z = \frac{U}{I} = \frac{350 \text{ V}}{35 \text{ A}} = \underline{\underline{10 \Omega}}$$

$$X_C = \sqrt{Z^2 - R^2} = \sqrt{10 \Omega^2 - 3,83 \Omega^2} = \underline{\underline{9,24 \Omega}}$$

$$X_L = 2 \cdot \pi \cdot f \cdot L \Rightarrow f = \frac{X_L}{2 \cdot \pi \cdot L} = \frac{9,24 \Omega}{2 \cdot \pi \cdot 58,80 \cdot 10^{-3} \text{ H}} = 25,0 \text{ Hz}$$