
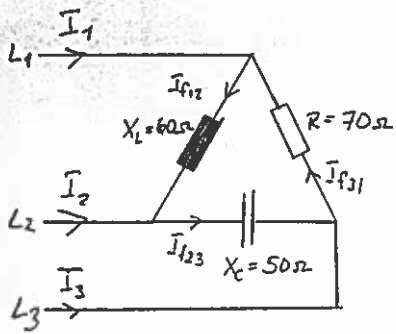


ppgave 8.3.1

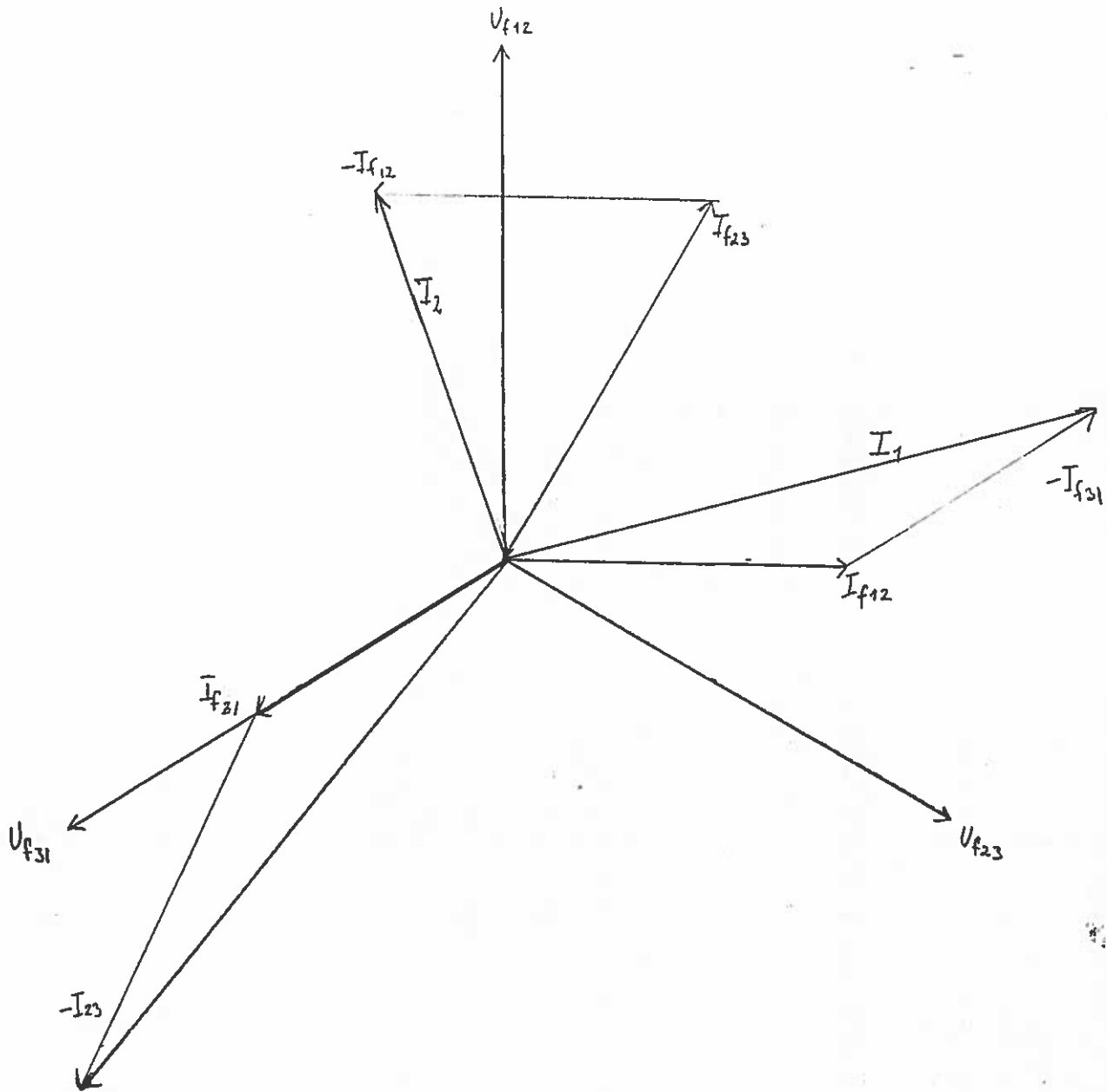

$$I_{12} = \frac{U_{f12}}{X_L} = \frac{220V}{60\Omega} = \underline{3,67A}$$


ANLEST: $I_1 = \underline{6,5A}$
 $I_2 = \underline{4,1A}$
 $I_3 = \underline{7,3A}$



$$I_{f31} = \frac{U_{f31}}{R} = \frac{220V}{70\Omega} = \underline{3,14A}$$

$$I_{f23} = \frac{U_{f23}}{X_C} = \frac{220V}{50\Omega} = \underline{4,4A}$$

IT Oppgave 8.3.2

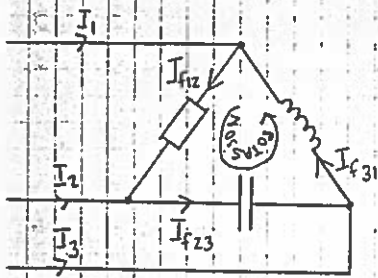

a) $I_{f12} = \frac{U_{f12}}{R} = \frac{230V}{100\Omega} = 2,3A$

$\beta_1 = \beta = 120^\circ - \varphi_3 = 120^\circ - 79,4^\circ = 40,6^\circ$


$I_1 = \sqrt{I_{f12}^2 + I_{f31}^2 - 2 \cdot I_{f12} \cdot I_{f31} \cdot \cos \beta_1}$

c) $I_1 = \sqrt{2,3A^2 + 2,83A^2 - 2 \cdot 2,3A \cdot 2,83A \cdot \cos 40,6^\circ} = 1,85A$

d) $P_{f12} = I_{f12} \cdot U_{f12} = 2,3A \cdot 230V = 529W$

$P_{TOT} = P_{f12} + P_{f23} + P_{f31} = 529W + 0 + 119,8W = 648,8W$

$1A = 2cm$

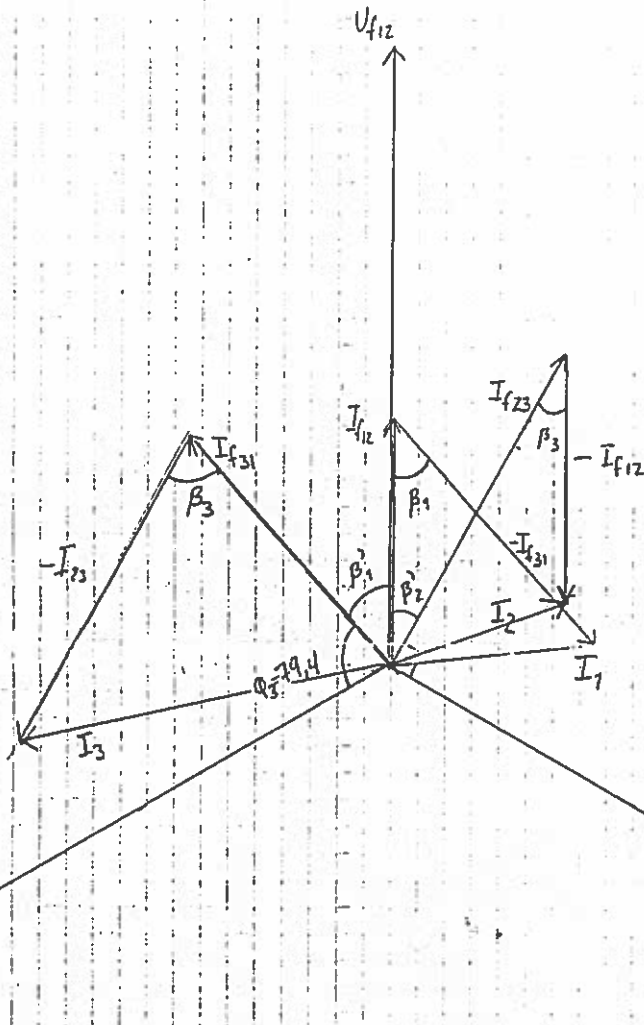

ROTASJONSRETNING

men etter
ningen

$\omega \cdot L = 80\Omega$

$R_s + jX_L = 15\Omega + j80\Omega = 81,4\Omega \angle \varphi_3 = 79,4^\circ$
 $\cos \varphi_3 = 0,184$

$I_{f31} = \frac{U_{f31}}{Z_s} = \frac{230V}{81,4\Omega} = 2,83A$

$\beta_1 + \beta_2 = 40,6^\circ + 30^\circ = 70,6^\circ$

$I_2 = \sqrt{I_{f31}^2 + I_{f23}^2 - 2 \cdot I_{f31} \cdot I_{f23} \cdot \cos \beta_2}$
 $\sqrt{2,83A^2 + 3,29A^2 - 2 \cdot 2,83A \cdot 3,29A \cdot \cos 70,6^\circ} = 3,56A$

$P_{f31} = I_{f31} \cdot U_{f31} \cdot \cos \varphi_3 = 230V \cdot 2,83A \cdot 0,184 = 119,8W$

Ideell kondensator:
Strømmen 90° foran
spenningen

$X_C = \frac{1}{\omega C} = 70\Omega$

a) $I_{f23} = \frac{U_{f23}}{X_C} = \frac{230V}{70\Omega} = 3,29A$

$\beta_2 = \beta_2 = 120^\circ - 90^\circ = 30^\circ$

c) $I_2 = \sqrt{I_{f23}^2 + I_{f12}^2 - 2 \cdot I_{f23} \cdot I_{f12} \cdot \cos \beta_2}$
 $\sqrt{3,29A^2 + 2,3A^2 - 2 \cdot 3,29A \cdot 2,3A \cdot \cos 30^\circ} = 1,75A$


$\alpha = 120^\circ - \varphi_3 = 120^\circ - 79,4^\circ = 40,6^\circ$

$\beta_2 = \alpha + \beta_1 = 40,6^\circ + 30^\circ = 70,6^\circ$


d) $P = 0W$ for en ideell kondensator

PGAVE 8.3.3

1.

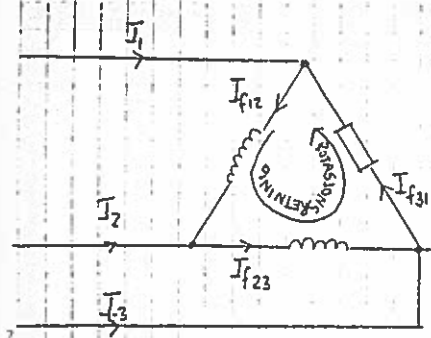

1cm = 25V
1cm = 2A

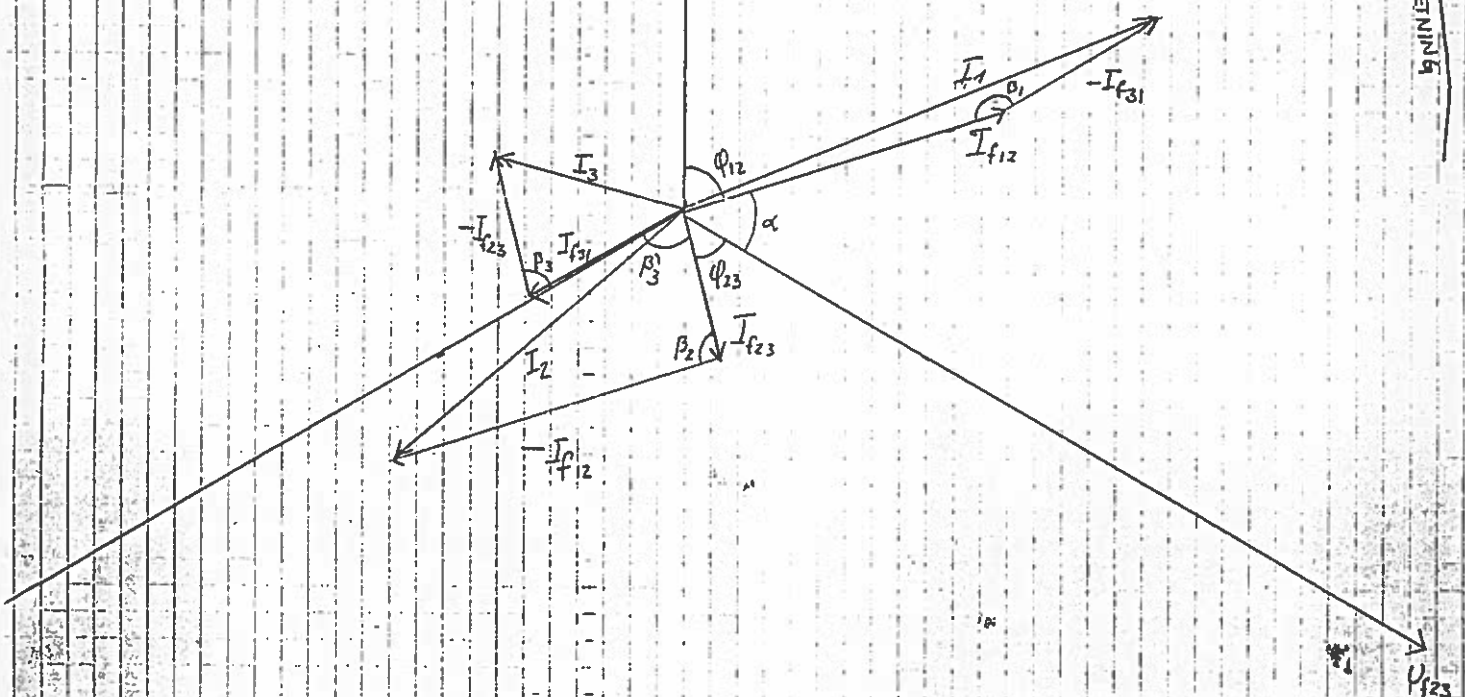

$$\frac{U_{f31}}{R_3} = \frac{400V}{60\Omega} = 6,67A$$

$$I_3 = \sqrt{I_{f23}^2 + I_{f31}^2 - 2 \cdot I_{f31} \cdot I_{f23} \cdot \cos \beta_3}$$

$$= \sqrt{6,67A^2 + 5,66A^2 - 2 \cdot 6,67A \cdot 5,66A \cdot \cos 75^\circ} = 7,5A$$

$$20^\circ - \phi_{23} = 120^\circ - 45^\circ = 75^\circ$$

$$P_{f31} = 400V \cdot 6,67A = 2668W$$

$$P_2 + P_{f23} + P_{f31} = 1605W + 1600W + 2668W = 5873W$$

FAS 12

a) $\bar{Z}_{12} = R_5 + jX_L = 10\Omega + j30\Omega = 31,6\Omega \quad \angle \phi_{12} = 71,6^\circ$
 $\cos \phi_{12} = 0,316$

$$I_{f12} = \frac{U_{f12}}{Z_{12}} = \frac{400V}{31,6\Omega} = 12,7A$$

Spole: strømmen etter spenningen

c) $I_1 = \sqrt{I_{f12}^2 + I_{f31}^2 - 2 \cdot I_{f12} \cdot I_{f31} \cdot \cos \beta_1}$
 $= \sqrt{12,7A^2 + 6,67A^2 - 2 \cdot 12,7A \cdot 6,67A \cdot \cos 168,4^\circ} = 19,3A$

$$\alpha = 120^\circ - \phi_{12} = 120^\circ - 71,6^\circ = 48,4^\circ$$

$$\beta_1 = 120^\circ + 48,4^\circ = 168,4^\circ$$

d) $P_{f12} = I_{f12} \cdot U_{f12} \cdot \cos \phi_{12} = 12,7A \cdot 400V \cdot 0,316 = 1605W$

FAS 2.3

a) $\bar{Z}_{23} = R_5 + jX_L = 50\Omega + j50\Omega = 70,7\Omega \quad \angle \phi_{23} = 45^\circ$
 $\cos \phi_{23} = 0,707$

$$I_{f23} = \frac{U_{f23}}{Z_{23}} = \frac{400V}{70,7\Omega} = 5,66A$$

spole: strømmen etter spenningen

c) $I_2 = \sqrt{I_{f23}^2 + I_{f12}^2 - 2 \cdot I_{f23} \cdot I_{f12} \cdot \cos \beta_2}$
 $I_2 = \sqrt{5,66A^2 + 12,7A^2 - 2 \cdot 5,66A \cdot 12,7A \cdot \cos 93,4^\circ} = 14,2A$

$$\alpha = 120^\circ - \phi_{12} = 120^\circ - 71,6^\circ = 48,4^\circ$$

$$\beta_2 = \alpha + \phi_{23} = 48,4^\circ + 45^\circ = 93,4^\circ$$


d) $P_{f23} = U_n \cdot I_n \cdot \cos \phi = 400V \cdot 5,66A \cdot \dots$

PPGANE 8.3.3

FAS 12


DEL 2

$I_{f12} = 6.67A$

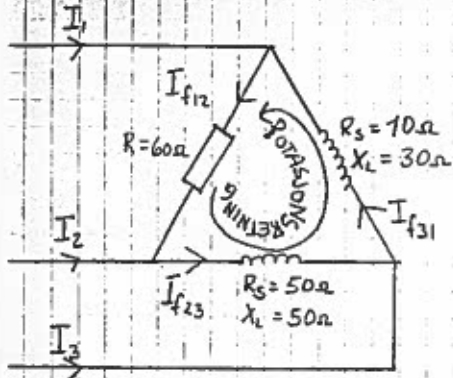

$1cm = 25V$

$1cm = 2A$

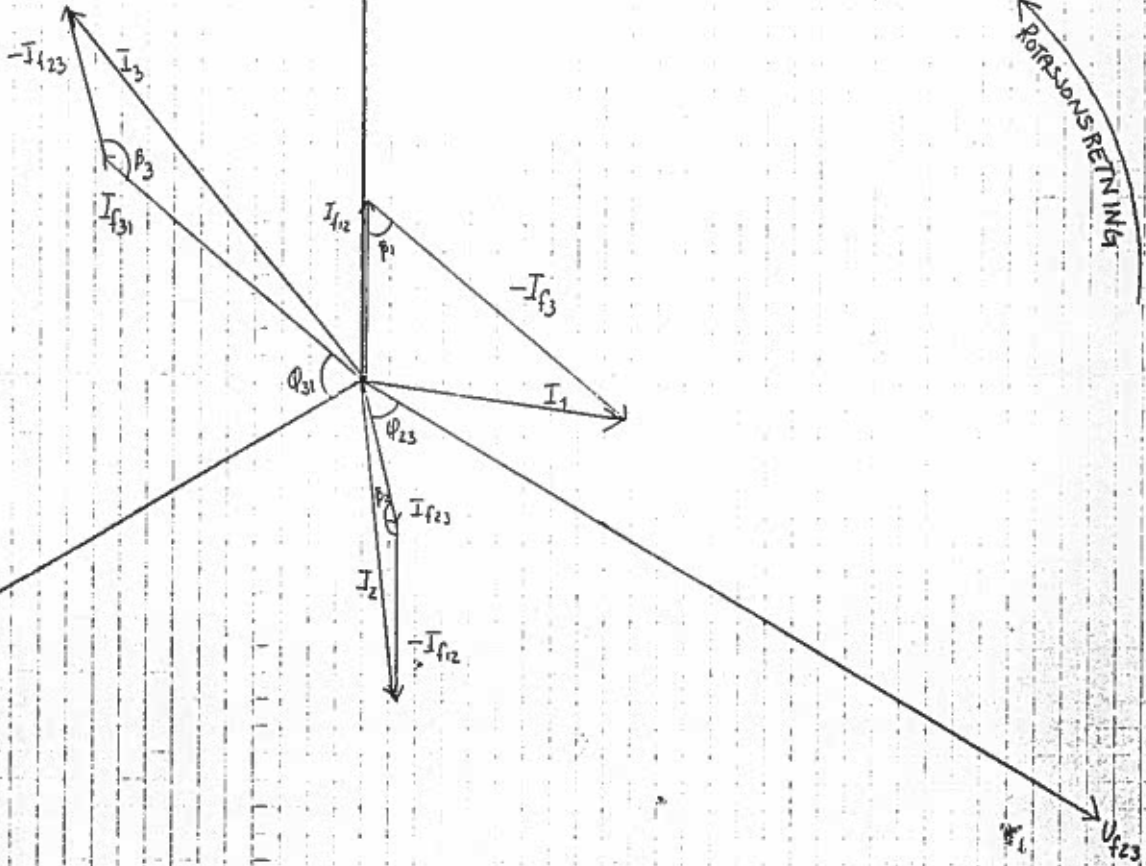

s 31

$= 12.7A \quad \angle \phi_{31} = 71.6^\circ \quad \cos \phi_{31} = 0.316$

FAS 23

$I_{f23} = 5.66A \quad \angle \phi_{23} = 45^\circ \quad \cos \phi_{23} = 0.707$