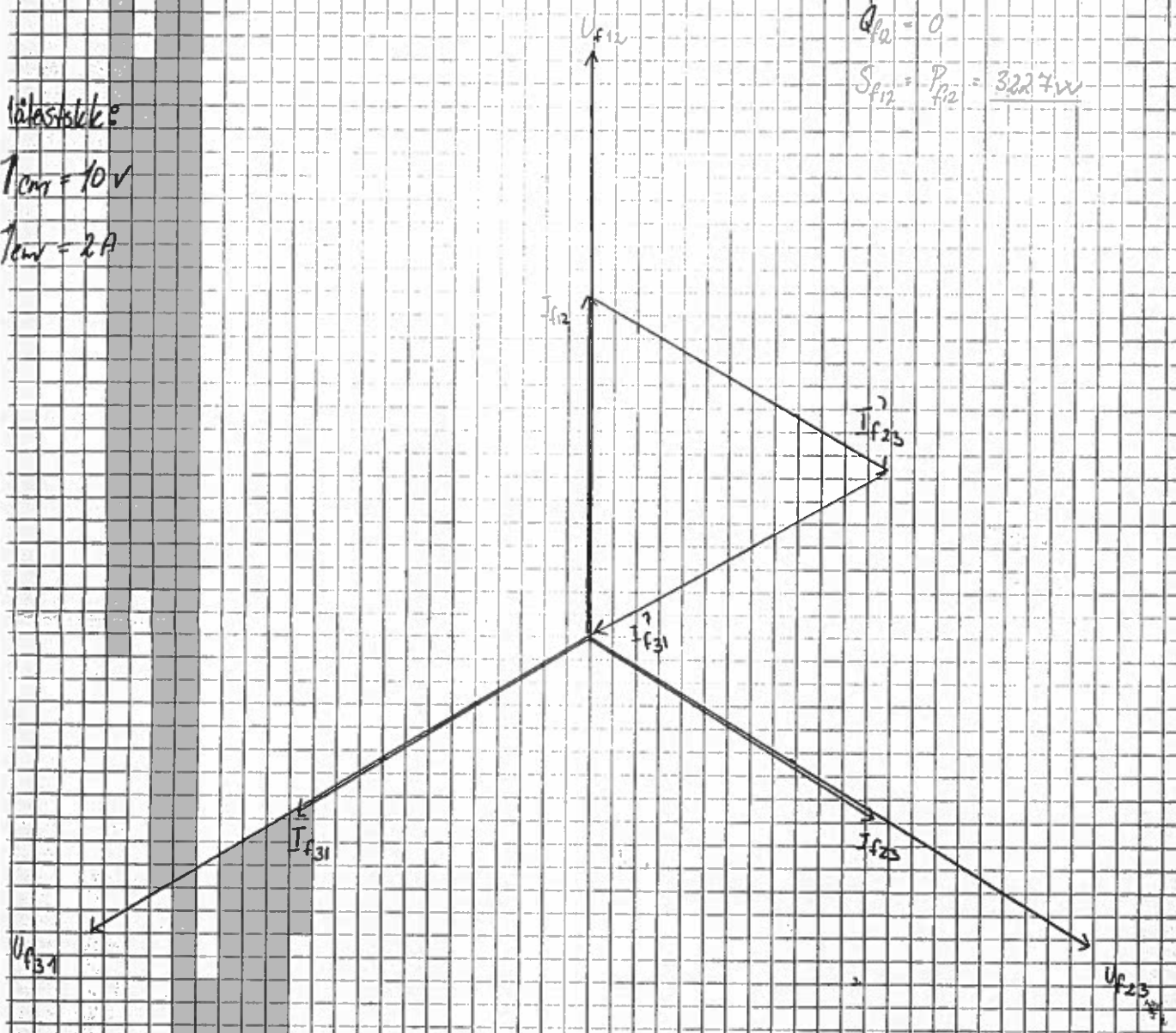


24.1

lasterstake:
 $U_{nom} = 10V$
 $I_{nom} = 2A$

g) $I_{f12} = \frac{U_{f12}}{R_{f12}} = \frac{220V}{15\Omega} = \underline{14.67A}$
 $P_{f12} = U_{f12} \cdot I_{f12} = 220V \cdot 14.67A = \underline{3227W}$
 $Q_{f12} = 0$
 $S_{f12} = P_{f12} = \underline{3227VA}$



$I_{f31} = I_{f12} = \underline{14.67A}$
 $P_{f31} = P_{f12} = \underline{3227W}$
 $S_{f31} = S_{f12} = \underline{3227VA}$

a) $I_{f23} = I_{f12} = \underline{14.67A}$
 $P_{f23} = P_{f12} = \underline{3227W}$
 $S_{f23} = S_{f12} = \underline{3227VA}$

Totala effekter:

$P = P_{f12} + P_{f23} + P_{f31} = 3227W + 3227W + 3227W = \underline{9682W}$ (6822-)
 $Q = 0$
 $S = P = \underline{9682VA}$

eller:
 $P = \sqrt{3} \cdot U \cdot I = \sqrt{3} \cdot 220V \cdot 14.67A$
 $= \underline{9655W}$

8.4.2


StkK:
= 20V
= 0.5A

a)


$$U_p = \frac{100V}{\sqrt{3}} = 230V$$

$$Z_p = 10\Omega + j50\Omega = 51.0\Omega \angle 78.7^\circ$$
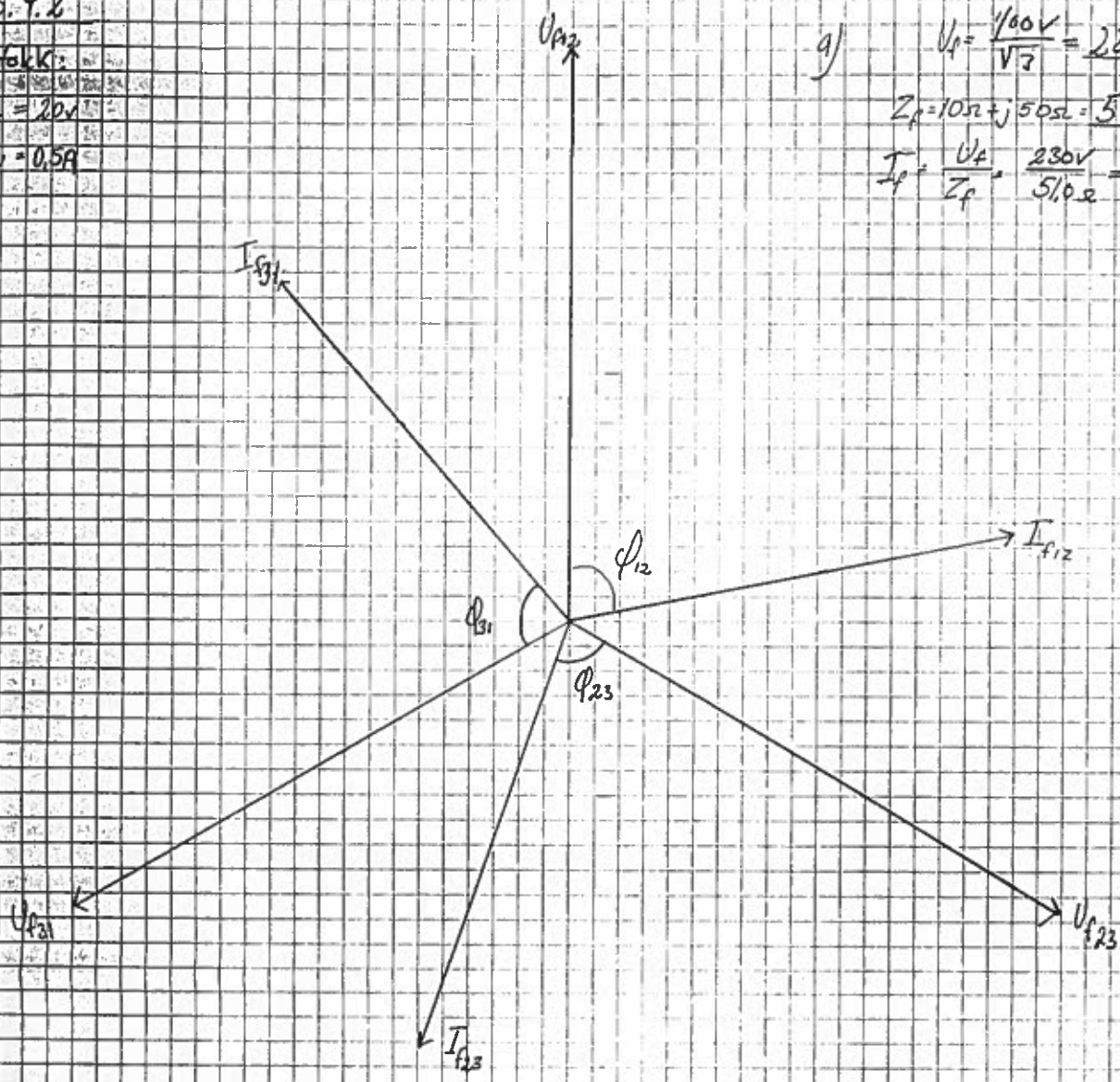
$$I_p = \frac{U_p}{Z_p} = \frac{230V}{51.0\Omega} = \underline{4.51A}$$



b)

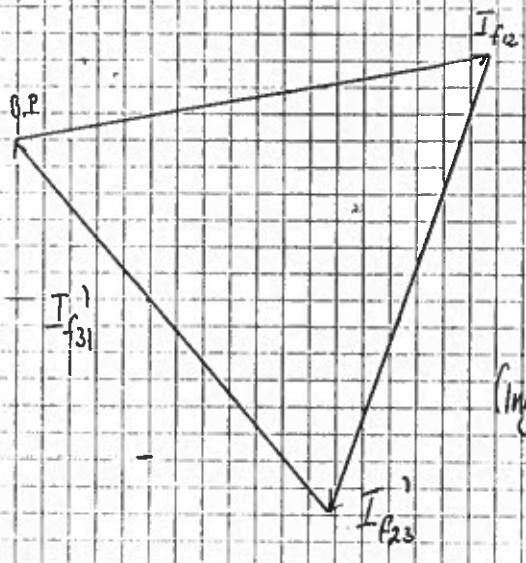

(Ingen strøm i nullleder)

Symmetri:

$$P = \sqrt{3} \cdot U \cdot I \cdot \cos \phi$$

$$P = \sqrt{3} \cdot 400V \cdot 4.51A \cdot \cos 78.7^\circ = \underline{612.3W}$$


$$S = \sqrt{3} \cdot U \cdot I$$

$$= \sqrt{3} \cdot 400V \cdot 4.51A = \underline{3124.6VA}$$

$$Q = \sqrt{3} \cdot U \cdot I \cdot \sin \phi$$

$$Q = \sqrt{3} \cdot 400V \cdot 4.51A \cdot \sin 78.7^\circ = \underline{3064VAR}$$

3.4.3

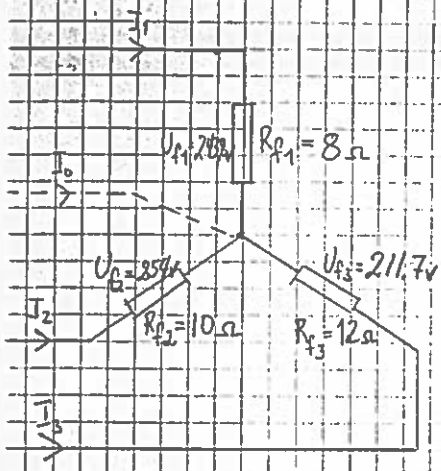


a)
$$I_{P1} = \frac{U_{P1}}{R_{P1}} = \frac{243.8V}{8 \Omega} = \underline{30.4A}$$

b)
$$P_{P1} = U_{P1} \cdot I_{P1} = 243.8V \cdot 30.4A = \underline{7412W}$$

stokk:

$l_{cm} = 20V$

$l_{cm} = 5A$

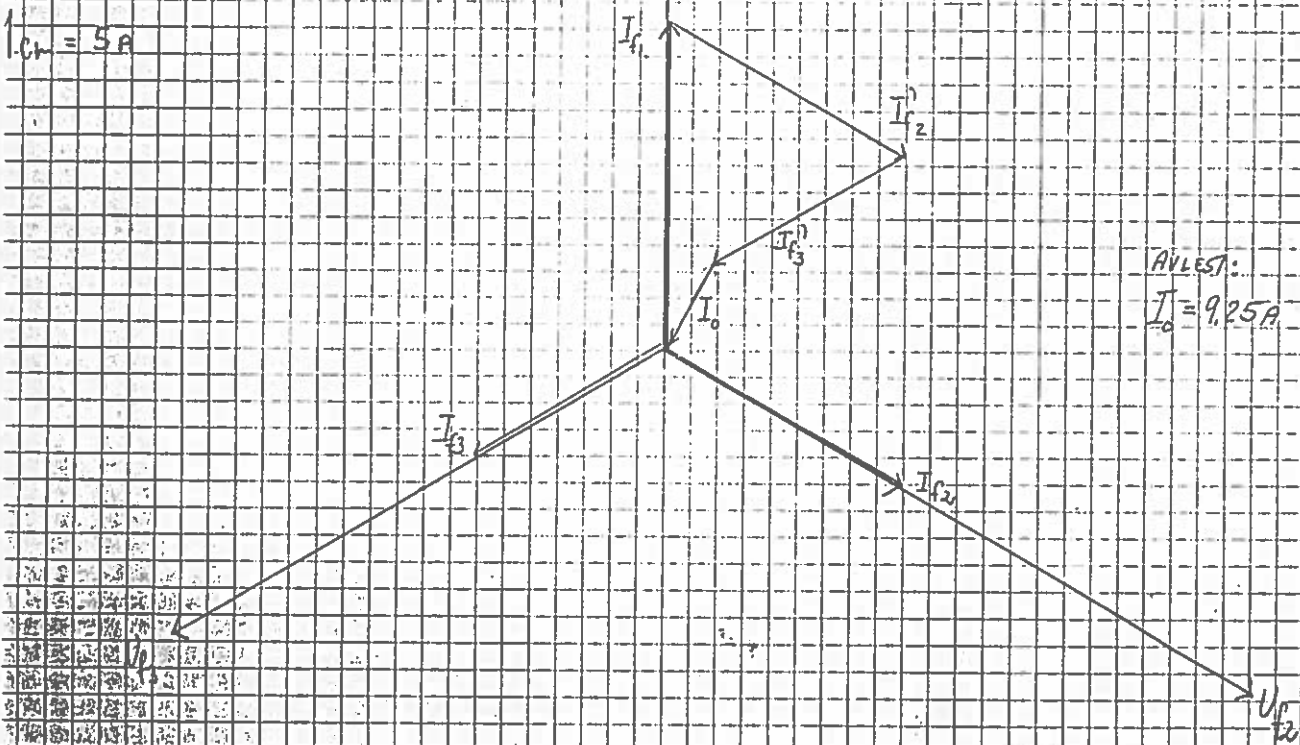

AVLEST:
 $I_0 = 9.25A$

a)
$$I_{P3} = \frac{U_{P3}}{R_{P3}} = \frac{211.7V}{12 \Omega} = \underline{17.6A}$$

b)
$$P_{P3} = U_{P3} \cdot I_{P3} = 211.7V \cdot 17.6A = \underline{3734W}$$

a)
$$I_{P2} = \frac{U_{P2}}{R_{P2}} = \frac{254.0V}{10 \Omega} = \underline{25.4A}$$

b)
$$P_{P2} = U_{P2} \cdot I_{P2} = 254.0V \cdot 25.4A = \underline{6350W}$$

$$P_{P1} + P_{P2} + P_{P3} = 7412W + 6350W + 3734W = \underline{17497W} = \underline{17.5kW}$$

8.4.14

Maßstab:

$1\text{cm} = 20\text{V}$
 $1\text{cm} = 0,5\text{A}$


Leistung:

$P = P_{f1} + P_{f2} + P_{f3} = 350,2\text{W} + 1429,3\text{W} + 179,7\text{W}$
 $= 1959,2\text{W}$

$S = S_{f1} + S_{f2} + S_{f3} = 583,2\text{VA} + 2380,5\text{VA} + 299,3\text{VA}$
 $= 3263\text{VA}$

$Q = Q_{f1} + Q_{f2} + Q_{f3} = 466,4\text{VAR} + 1903,6\text{VAR} + 239,3\text{VAR}$
 $= 2609,3\text{VAR}$

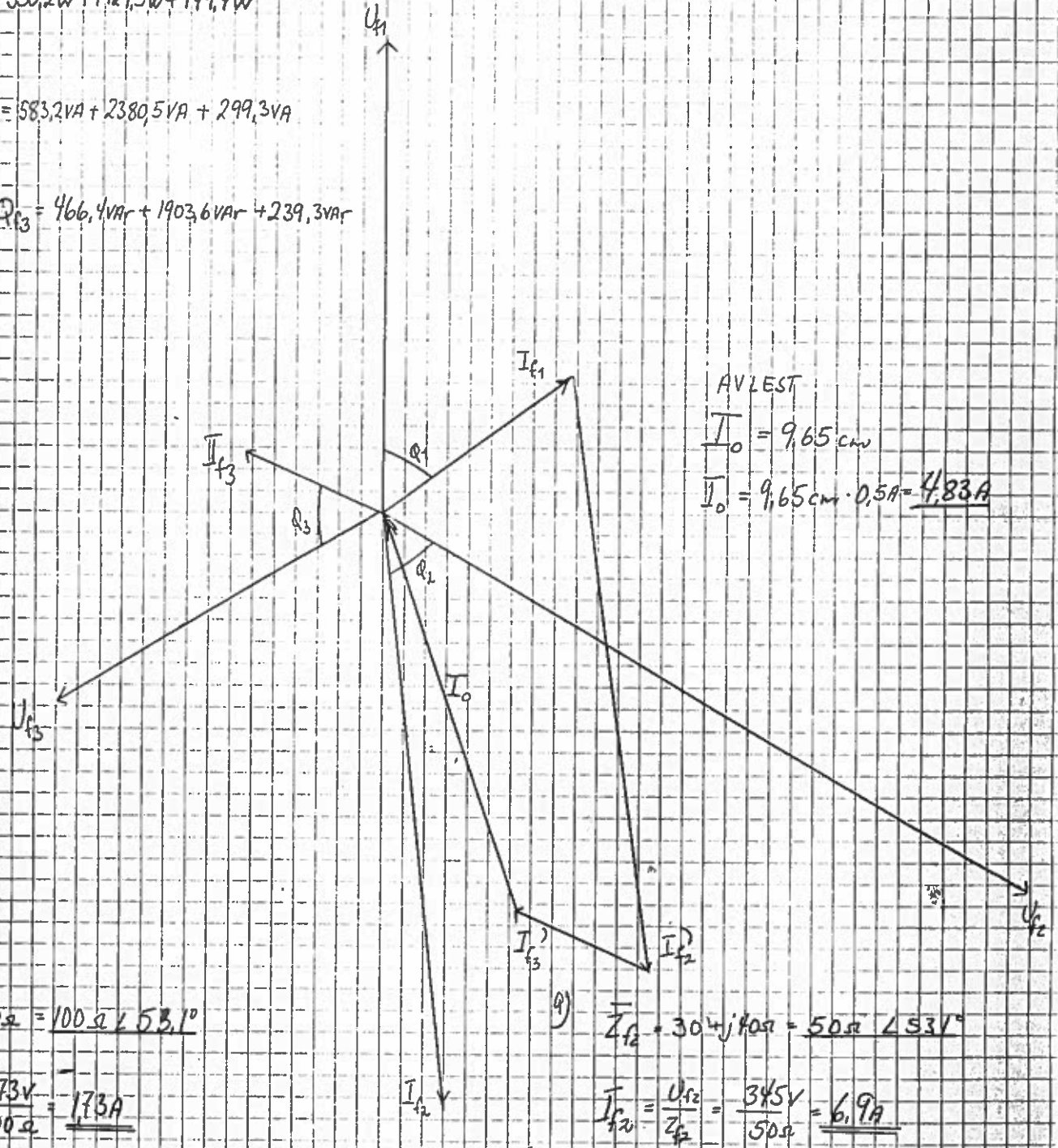a) $\bar{Z}_{f1} = 48\Omega + j64\Omega = 80\Omega \angle 53,1^\circ$
 $I_{f1} = \frac{U_{f1}}{Z_{f1}} = \frac{216\text{V}}{80\Omega} = 2,7\text{A}$
 c) $P_{f1} = U_{f1} \cdot I_{f1} \cdot \cos\phi_1 = 216\text{V} \cdot 2,7\text{A} \cdot \cos 53,1^\circ = 350,2\text{W}$
 $S_{f1} = U_{f1} \cdot I_{f1} = 216\text{V} \cdot 2,7\text{A} = 583,2\text{VA}$
 $Q_{f1} = U_{f1} \cdot I_{f1} \cdot \sin\phi_1 = 216\text{V} \cdot 2,7\text{A} \cdot \sin 53,1^\circ = 466,4\text{VAR}$



AVLEST
 $I_0 = 9,65\text{cm}$
 $I_0 = 9,65\text{cm} \cdot 0,5\text{A} = 4,83\text{A}$

$Z_{f3} = 60\Omega + j80\Omega = 100\Omega \angle 53,1^\circ$

$I_{f3} = \frac{U_{f3}}{Z_{f3}} = \frac{173\text{V}}{100\Omega} = 1,73\text{A}$

$P_3 = U_{f3} \cdot I_{f3} \cdot \cos\phi_3 = 173\text{V} \cdot 1,73\text{A} \cdot \cos 53,1^\circ = 179,7\text{W}$

$S_3 = U_{f3} \cdot I_{f3} \cdot \cos\phi_3 = 173\text{V} \cdot 1,73\text{A} = 299,3\text{VA}$

$Q_3 = U_{f3} \cdot I_{f3} \cdot \sin\phi_3 = 173\text{V} \cdot 1,73\text{A} \cdot \sin 53,1^\circ = 239,3\text{VAR}$

a) $\bar{Z}_{f2} = 30\Omega + j40\Omega = 50\Omega \angle 53,1^\circ$

$I_{f2} = \frac{U_{f2}}{Z_{f2}} = \frac{345\text{V}}{50\Omega} = 6,9\text{A}$

c) $P_{f2} = U_{f2} \cdot I_{f2} \cdot \cos\phi_2 = 345\text{V} \cdot 6,9\text{A} \cdot \cos 53,1^\circ = 1429,3\text{W}$

$S_{f2} = U_{f2} \cdot I_{f2} = 345\text{V} \cdot 6,9\text{A} = 2380,5\text{VA}$

$Q_{f2} = U_{f2} \cdot I_{f2} \cdot \sin\phi_2 = 345\text{V} \cdot 6,9\text{A} \cdot \sin 53,1^\circ = 1903,6\text{VAR}$